

*Arnav Goyal*

# Digital Design

SELF STUDY

## *Preface*

The purpose of this document is to act as a comprehensive note for my understanding on the subject matter. I may also use references aside from the lecture material to further develop my understanding, and these references will be listed here.

This document should eventually serve as a standalone reference for learning or review of the subject matter. There is also a lot of organization within these documents, please refer to the table of contents within your PDF viewer for ease of navigation.

## *References*

- Provided Course Materials from ECE 2277, ECE 3375
- Digital Design with an Introduction to the Verilog HDL - 5e - M. Mano, D. Ciletti
- Verilog Complete Tutorial - VLSI Point (YouTube Link)

# *Finite State Machines*

A **finite state machine** or<sup>1</sup> (**FSM**) is a system that can be in a finite number of **states**, accept a finite set of **inputs**, producing a finite state of **outputs**.

<sup>1</sup> Sometimes an FSM is called a Finite State Automaton

- Listing these states, the possible transitions between states based on the input, and the conditions required for each possible output, provides a complete function description of an FSM.

A FSM is a general concept, a mathematical concept. However, when dealing with a specific subset of then called **deterministic FSMs**, we can actually implement them with sequential circuits.

- An FSM is **deterministic** if every combination of current state and input results in only one transition (no probabilistic transitions).

## *Mathematical Formalism*

There are two types of FSMs. A **Mealy** and a **Moore** FSM.

- The output of a Moore FSM depends on only the state it is currently in.
- The output of a Mealy FSM depends on transitions between states.

Lets make things more organized by introducing some basic mathematical notation to this.

- Let the set of all possible states in an FSM be denoted by  $Q$ , lets also call the starting state  $Q_0$
- Let the set of all possible inputs be called  $I$
- Let the transition function be denoted  $\delta(Q, I)$ , it determines the next state as a function of the current state and next input, we say:  $\delta : Q \times I \mapsto Q$
- Let the output function be given by  $f(\cdot)$ , it determines the output as a function of something.

This means that any FSM  $M$  can be described by the following basic description<sup>2</sup>

$$M = (Q, I, Q_0, \delta, f)$$

We can differentiate mathematically between Mealy and Moore FSMs through the description of their output functions. Let the set  $O$  be the set of all possible outputs.

- A Moore FSMs output function is defined<sup>3</sup> as  $f : Q \mapsto O$ .
- A Mealy FSMs output function is defined<sup>4</sup> as  $f : \delta \mapsto O$

<sup>2</sup> Here the functions are written as variables for clarity, we also probably cant define these functions in any way other than a truth/state table. For now just assume that they can.

<sup>3</sup> A Moore FSMs output depends ONLY on its current state

<sup>4</sup> A Mealy FSMs current output depends on the SPECIFIC transition it is experiencing

# Clock Domain Crossing

## Clock Domains & Metastability

So far we've only discussed **synchronous** circuits<sup>5</sup>. In the real world, it is extremely common to have **asynchronous** circuits<sup>6</sup>. Consider some circuit  $C$  with two design blocks  $C_1, C_2 \subseteq C$

- we say that the circuit is synchronous if the only clock within  $C$  is  $f_1$  or derivatives<sup>7</sup> of  $f_1$
- we say that the circuit is asynchronous if there are multiple clocks - if  $C_1$  is clocked by  $f_1$ , and  $C_2$  clocked by  $f_2$

A problem occurs<sup>8</sup> when trying to send data from  $C_1$  to  $C_2$ , we are trying to send data at some frequency  $f_1$ , and trying to sample it on some frequency  $f_2$ . Sending data through different clock domains like this is called **clock domain crossing** or (**CDC**)

Whenever this occurs, the data we are trying to send has the possibility of becoming **metastable**.

- When a signal is metastable, it means that it isn't a well defined 0 or 1.

<sup>5</sup> circuits that share the same clock.

<sup>6</sup> circuits with multiple clocks

<sup>7</sup> Any clocks with constant phase relationships, such as  $f_1/2, f_1/4$ , etc.

<sup>8</sup> This is the problem with Clock Domain Crossing (CDC)

- Metastability arises from violating the **setup and hold times**<sup>9</sup> of a flip-flop.

### *Crossing Clock Domains*

When crossing clock domains, metastability arises, it is not possible to completely remove metastability from a design, but with the proper procedures we can reduce the chances of it happening.

- A measure of metastability can be approximated through the notion of **mean time between failures** also (**MBTF**)<sup>10</sup>
- We *deal* with metastability by increasing the MBTF as much as we can through the use of some **CDC techniques**.
- A metastable signal entering a flip flop will either produce a metastable output, or a well defined 0 or 1. There is no way to tell, as this is probabilistic in nature.

Now we will learn the most common techniques to deal with CDC

- The *n*-flop synchronizer
- Handshake Synchronizer<sup>11</sup>
- Asynchronous FIFO (Queue)<sup>12</sup>

These are extremely complex circuits, so we will only be learning about the first method.

<sup>9</sup> Setup time  $t_s$  refers to the amount of time the input must be stable before the clock edge arrives. Hold time  $t_h$  refers to the amount of time the input must be stable after the clock edge arrives

<sup>10</sup> This is an estimate due to the probabilistic nature of metastability. The below equation is provided by cadence's CDC paper

$$\text{MBTF} = \frac{\exp(k_1 t_{\text{meta}})}{k_2 \cdot f_{\text{clk}} \cdot f_{\text{data}}}$$


<sup>11</sup> works through a 'request' and 'acknowledge' mechanism

<sup>12</sup> tx writes into the queue, and rx reads from the queue.

### *n*-Flop Synchronizer

The most common way to deal with CDC is to construct an *n*-flop synchronizer<sup>13</sup>. The circuit of 2-flop synchronizer looks like this.

<sup>13</sup> usually *n* is 2 or 3

 

It's easy to see how this circuit can be arbitrarily extended to contain *n*-flops. Adding a flop flop to the chain increased MBTF, but also adds latency to our design.

- This design works because even if the data becomes metastable after propagating through B1, it has another clock cycle to settle and become a well defined 0 or 1 before propagating through B2.
- Each additional flip-flop in the chain gives the (possibly) metastable signal more time to settle before being sent out.

# *Reset Domain Crossing*

## *Reset Domains & Metastability*

Consider a circuit with many different flip-flops. We define a **reset domain** as the set of any flip flops that share the same reset signal *rstn*.

- The reset signal guarantees that the data output is 0 during its **assertion**.
- Metastability can only occur during the **deassertion** of a reset signal.